

Adding 2 bits

Understanding the problem:

Consider the two bits 0, 1 and add them together
in all possible combinations

a	0	0	1	1
b	0	1	0	1
c _{out}	0	0	0	1
Sum	0	1	1	0

Every addition produces a half-sum (s) and a carry out (c_{out}).

Let us now reorder our information in the form of two
Truth Tables:

a	b	s
0	0	0
0	1	1
1	0	1
1	1	0

≡ XOR

a	b	c _{out}
0	0	0
0	1	0
1	0	0
1	1	1

≡ AND


Thus adding a to b ($a + b$) can be done with logic gates!

$$\text{Sum} = a \oplus b$$

$$\text{Cout} = a \cdot b$$

ADDING IS BEING
EXPRESSED USING
LOGIC

The logic circuit to add 2 bits is thus:

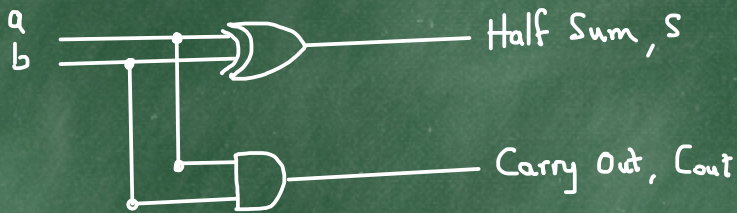

This circuit is called a half-adder

Looking More closely at the 'Carry' process

Decimal Example : add 796 to 248


$$\begin{array}{r} 796 \\ + 248 \\ \hline 1044 \end{array}$$

We see that if we wish to perform multidigit addition, we need to add 3 things in each step: a Carry-in, a Summand, and an augend.

Each step results in a Sum and a Carry-out (which becomes the Carry-in to the next, higher-order addition)

$$\begin{array}{r} \text{Carry-out } 1 \rightarrow \\ 80 \\ + 6 \\ \hline 4 \end{array}$$

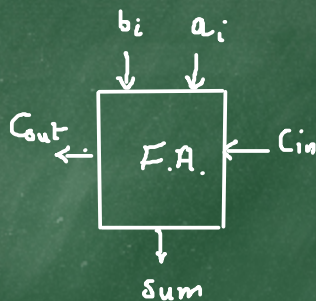Labels for the addition step:
6 ← Augend — a_i
80 ← Summand — b_i
1 ← Carry-in — C_{in}
4 ← Sum



We call this component a
Full-Adder (F.A.)


We Can Combine full-adders to make multidigit ADDERS

In general

$$\begin{array}{r}
 a_{n-1} \quad a_{n-2} \quad \dots \quad a_2 \quad a_1 \quad a_0 \\
 b_{n-1} \quad b_{n-2} \quad \dots \quad b_2 \quad b_1 \quad b_0 \quad 0 \\
 \hline
 s_{n-1} \quad s_{n-2} \quad \dots \quad s_2 \quad s_1 \quad s_0
 \end{array}$$

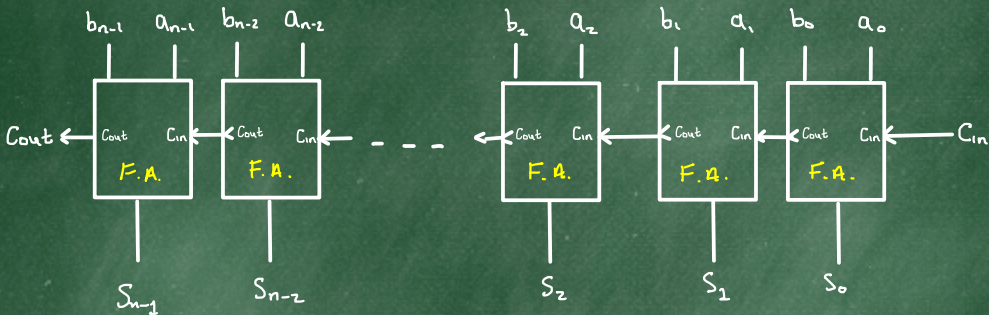
Example

$$\begin{array}{r}
 a_{n-1} \quad a_{n-2} \quad a_2 \quad a_1 \quad a_0 \\
 1 \quad 1 \quad 1 \quad 0 \quad 1 \quad 1 \quad 0 \\
 b_{n-1} \quad b_{n-2} \quad b_2 \quad b_1 \quad b_0 \quad 0 \\
 1 \quad 0 \quad 1 \quad 1 \quad 1 \quad 1 \quad 1 \quad 0 \\
 \hline
 1 \quad 0 \quad 1 \quad 1 \quad 0 \quad 1 \quad 0 \quad 0 \quad 0 \\
 s_{n-1} \quad s_{n-2} \quad s_2 \quad s_1 \quad s_0
 \end{array}$$



An n-bit multidigit Binary Ripple-Carry Adder.

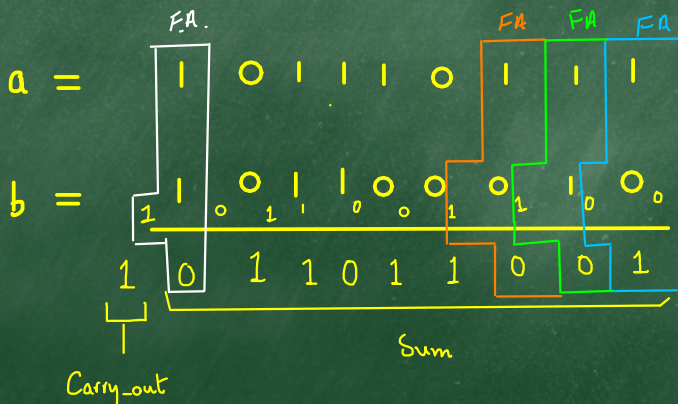The Carry **ripples** through the circuit, giving the device its name.



Building a Logic Circuit to Implement a Full-ADDER

Construct a Truth Table for a Full-ADDER by tabulating all possible combinations of inputs against their associated outputs

Inputs			Outputs		
C_{in}	a	b	Sum	C_{out}	
0	0	0	0	0	$C_{in} = 0$ $Sum = a \oplus b$ $C_{out} = a \cdot b$
0	0	1	1	0	
0	1	0	1	0	
0	1	1	0	1	
1	0	0	1	0	$C_{in} = 1$ $Sum = a \odot b$ $C_{out} = a + b$
1	0	1	0	1	
1	1	0	0	1	
1	1	1	1	1	

Later, we will learn a mechanistic way of creating equation and circuits from truth tables.

For now, we are going to create a circuit by intuition and pattern matching (i.e., comparing what we see with what we already know)

In doing this,

we can consider this truth table as consisting of 2

parts: Part 1, where $C_{in} = 0$ and Part 2, where $C_{in} = 1$.